

# Power Factor Improvement

State Energy Assessment Workshop

By:

DTE Energy Partnership & Services

# Power Factor (pf) Correction

---

- Why is it needed
- How do we correct it
- How does it affect electrical bills

# Types of loads

---

□ There are three categories

■ Resistive



Ohms  $\Omega$

■ Inductive




Henry H

■ Capacitive




Farad F




# Resistive Load

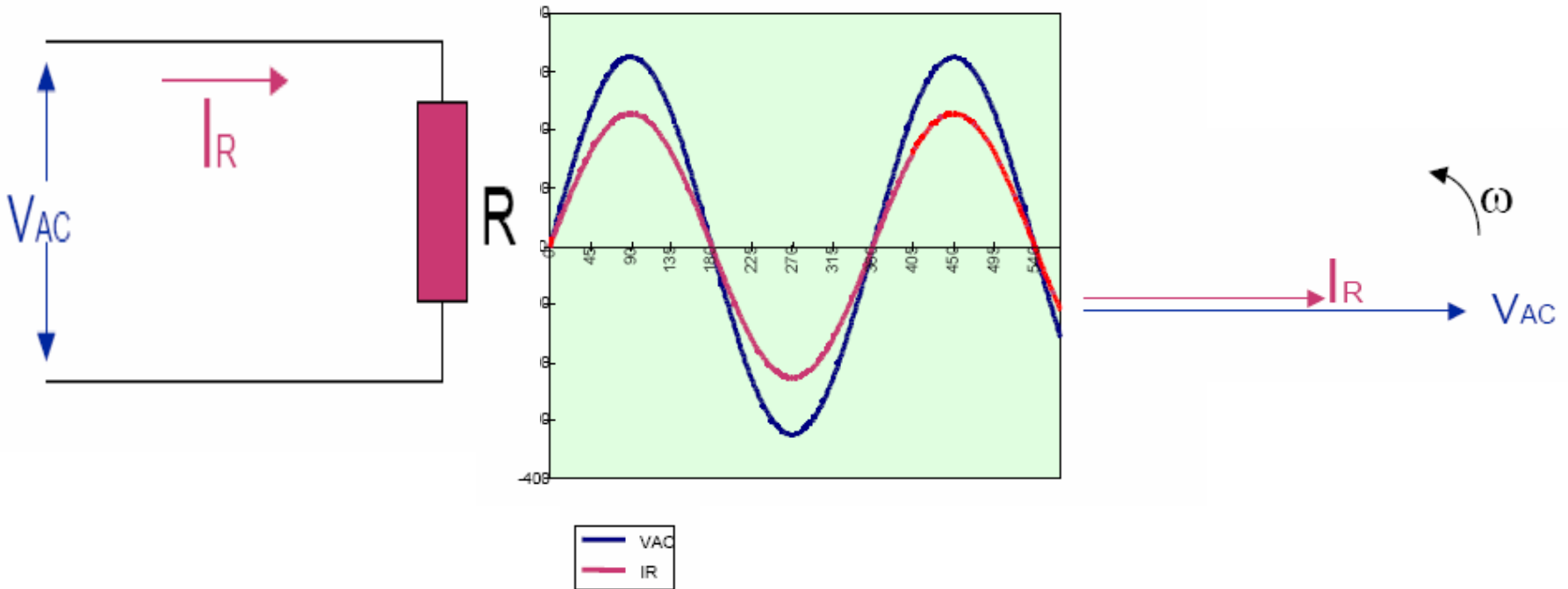

# Inductive Load

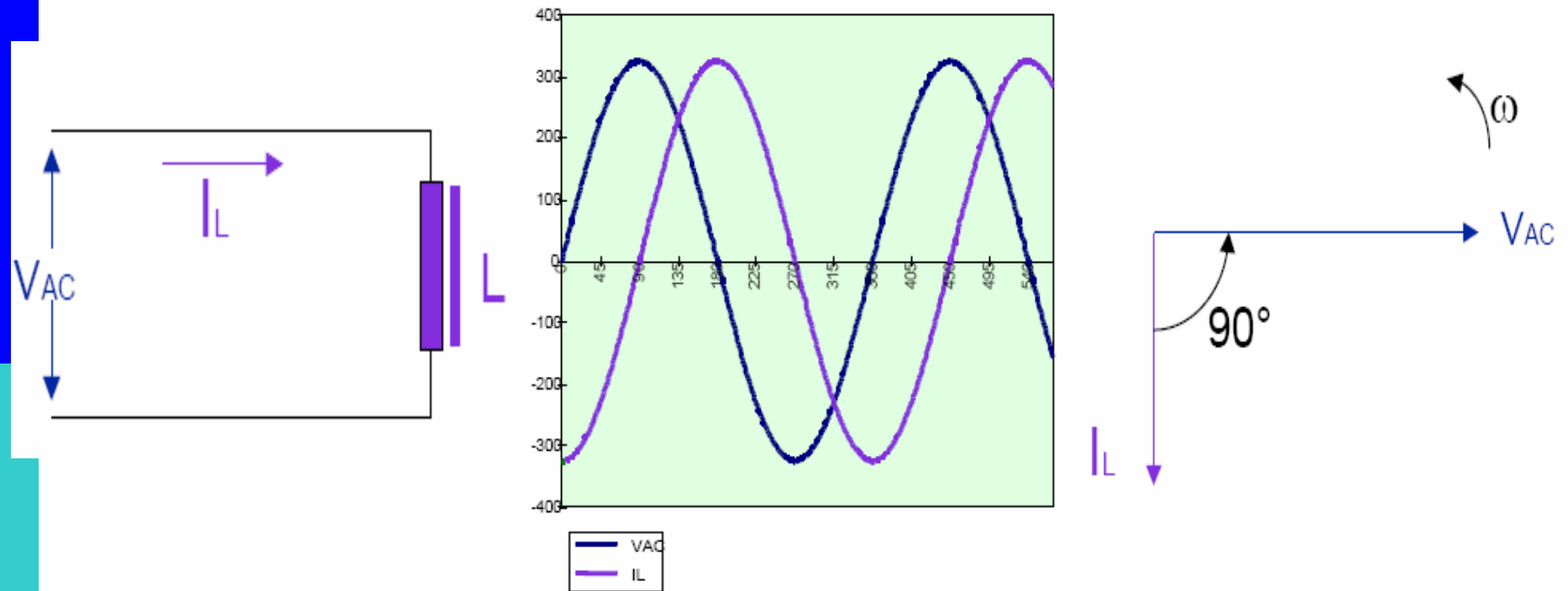

# Capacitive Load

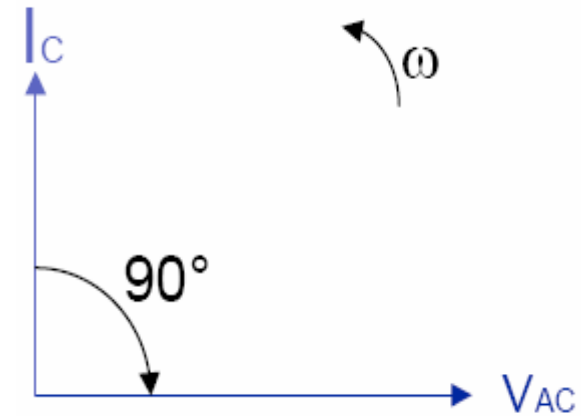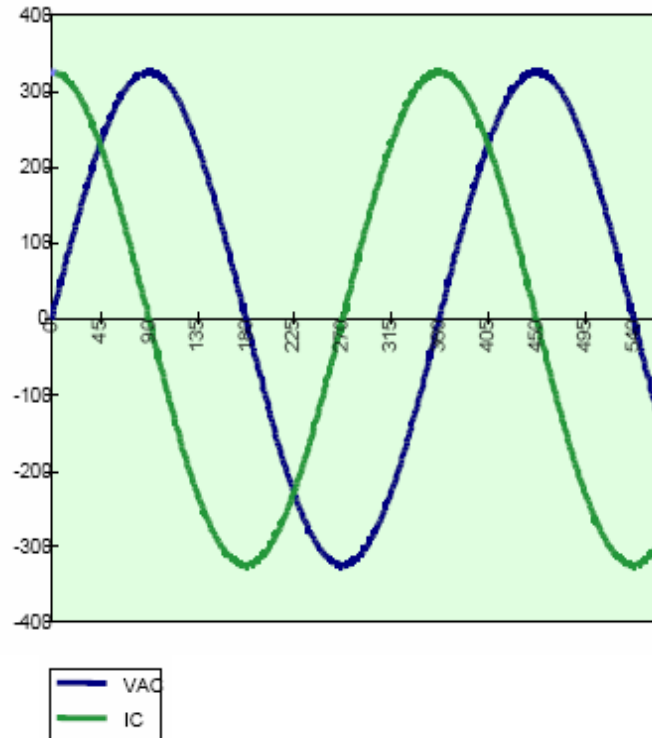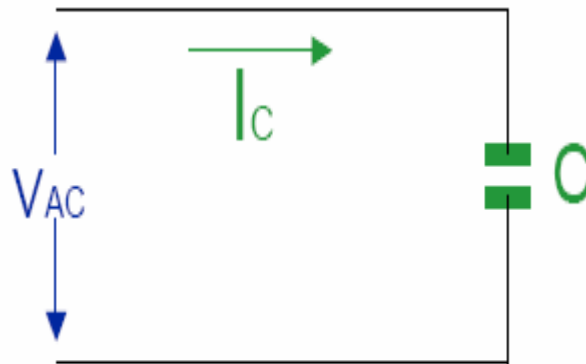

# Power

---


- Real Power (P)
  - Is the actual amount of power being used or dissipated in a circuit; measured in watts.
  - It is a function of a circuit's resistance R;  $P = I^2R$
- Reactive Power (Q)
  - Is the amount of absorbed/returned power by the reactive loads (KVAR)
  - It is a function of a circuit's reactance X;  $Q = I^2X$
- Apparent Power
  - Is the combination of reactive power and true power; measured in (VA).
  - It is a function of a circuit's impedance Z;  $S = I^2Z$

# Real Loads

- ❑ Main industrial loads can all be considered to be a combination between resistive and inductive loads

- ❑ Current always lags

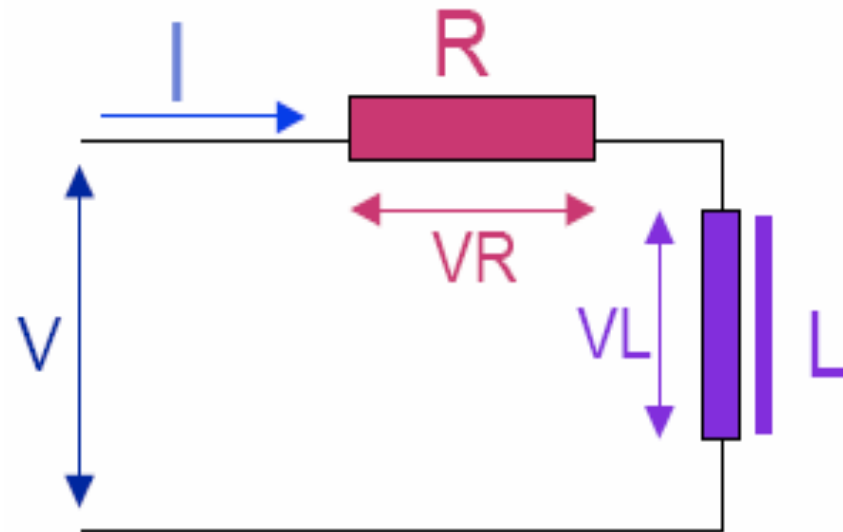Voltage by some  
angle except in total  
resistive loads






# Power Factor

---


- Is a measure of how effectively the current is being converted into useful work output
- Is a good indicator of the effect of the load current on the efficiency of the supply system.

# Power Factor

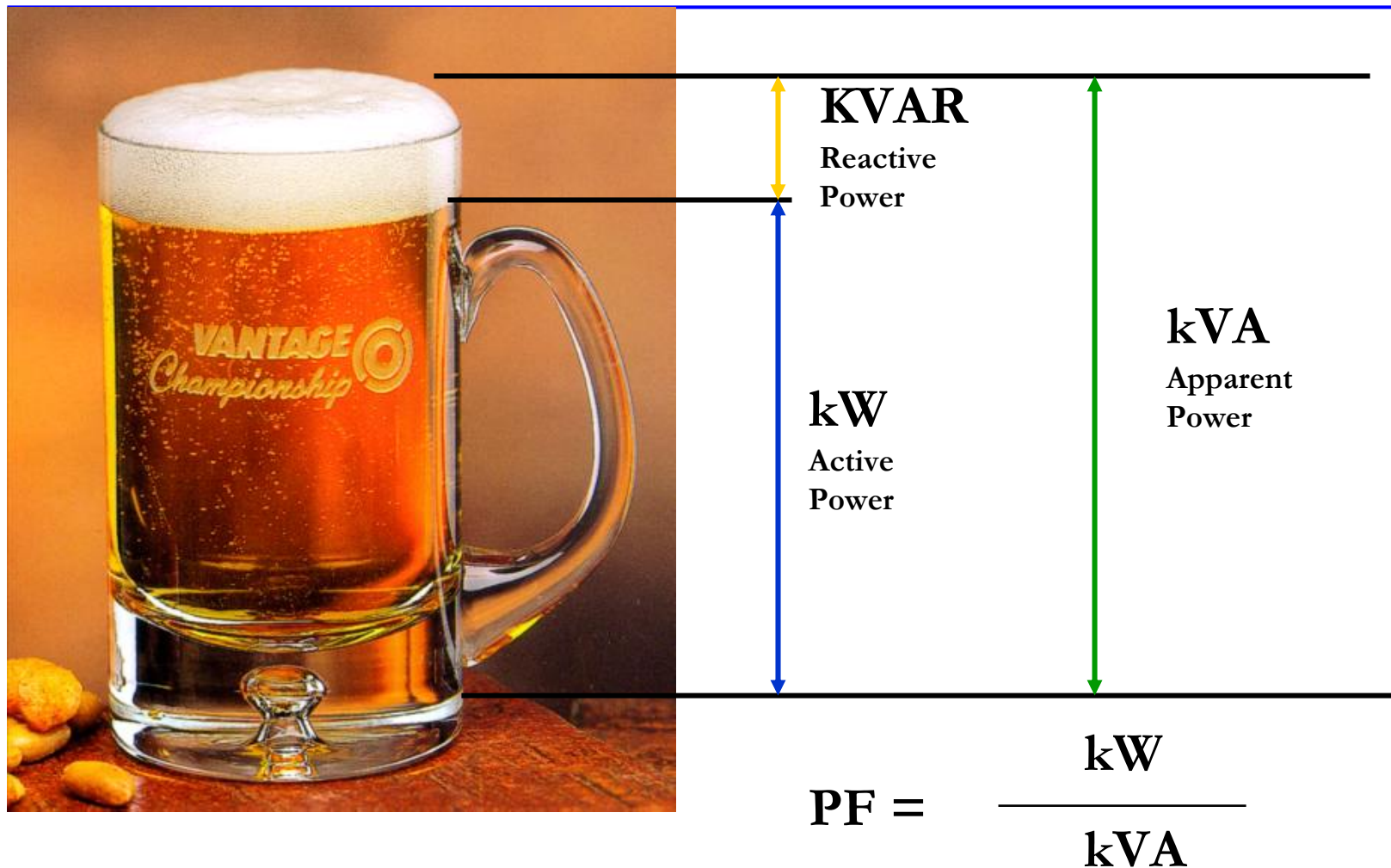
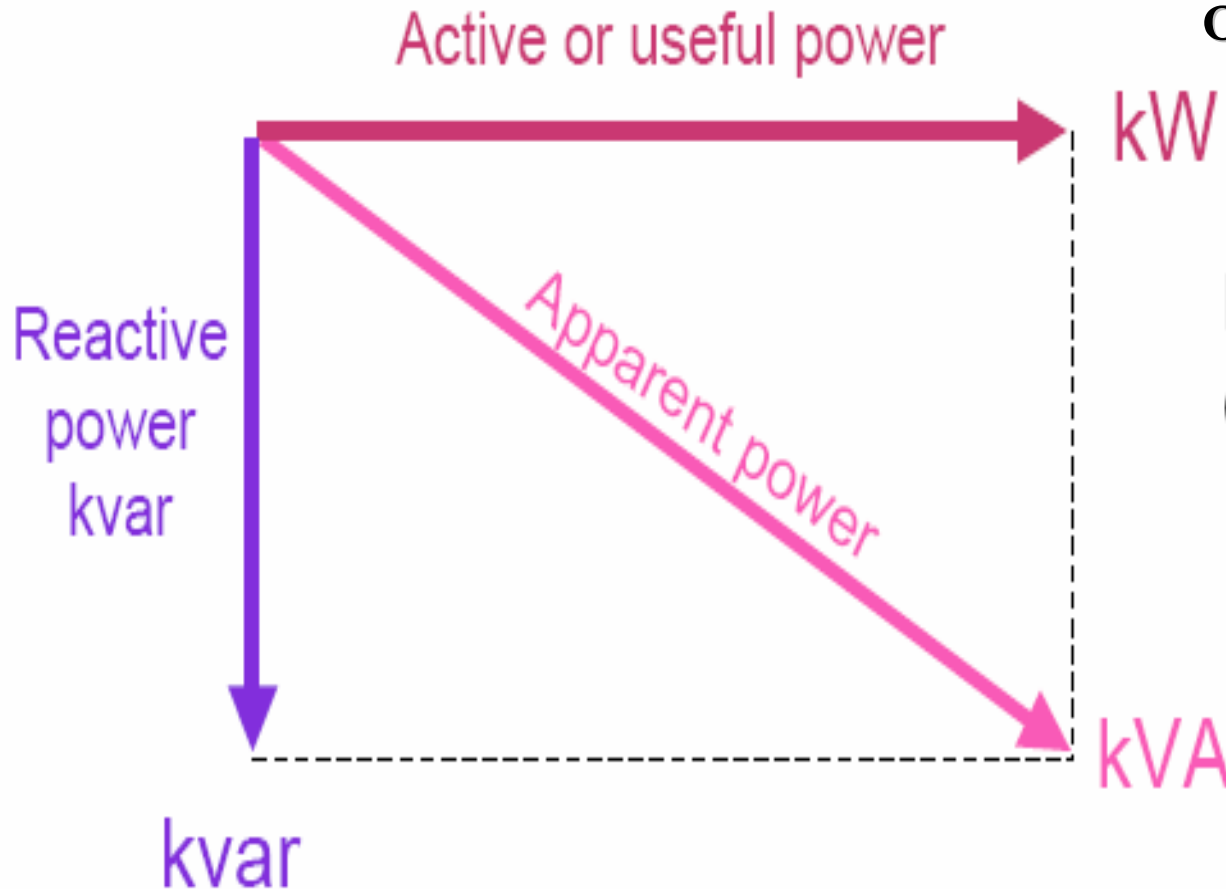
# Power:

Power Factor is a  
measure of Efficient  
Output/Input



Power factor  
 $\cos \phi = \text{kW} / \text{kVA}$

# Basic Concepts

$$\cos \Phi = \frac{\text{kW}}{\text{kVA}}$$




$$\sin \Phi = \frac{\text{kvar}}{\text{kVA}}$$

$$\text{kVA} = \sqrt{\text{kW}^2 + \text{kvar}^2}$$

$$\cos \Phi = \frac{\text{kW}}{\sqrt{\text{kW}^2 + \text{kvar}^2}}$$

$$\tan \Phi = \frac{\text{kvar}}{\text{kW}}$$
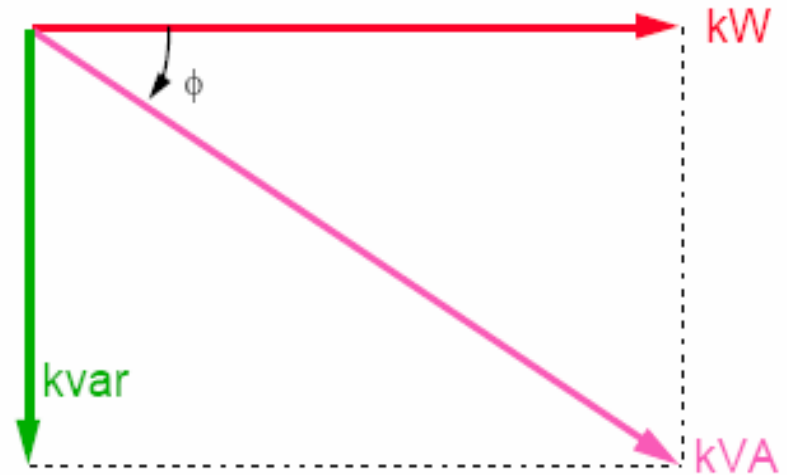
$$\text{kvar}_{\text{arc}} = \text{kW}(\tan \Phi_1 - \tan \Phi_2)$$





# How to Improve Power Factor

---


- ❑ Using the correct sized motor for a particular job
- ❑ Shutting off unused motors
- ❑ Installing a capacitor.

# Adding a Capacitor


## □ Capacitor connection

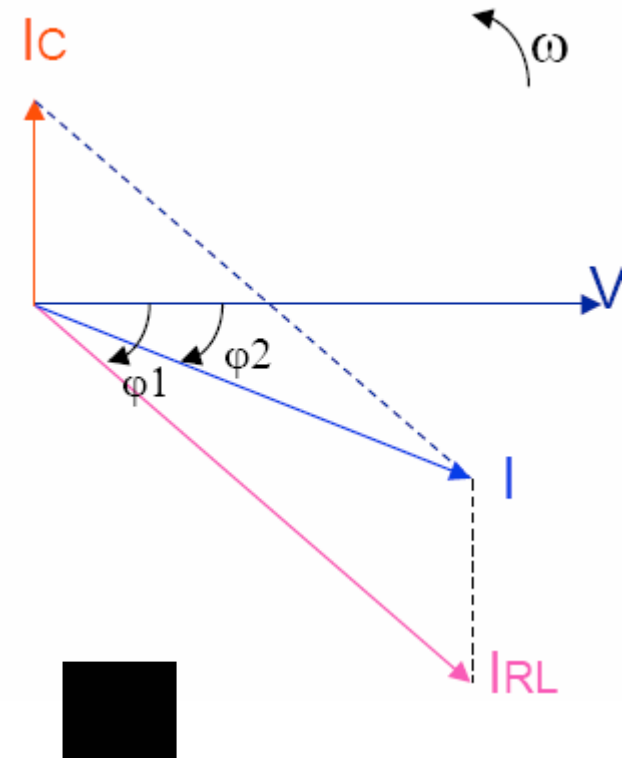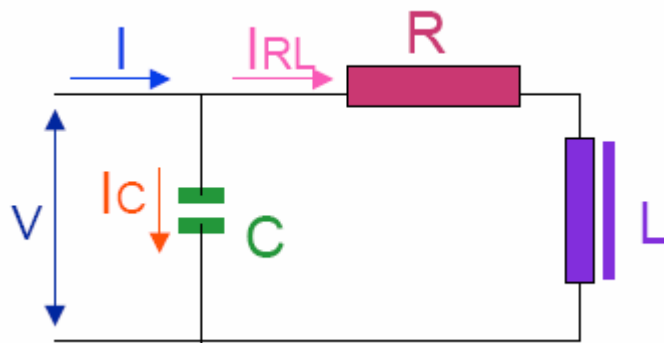

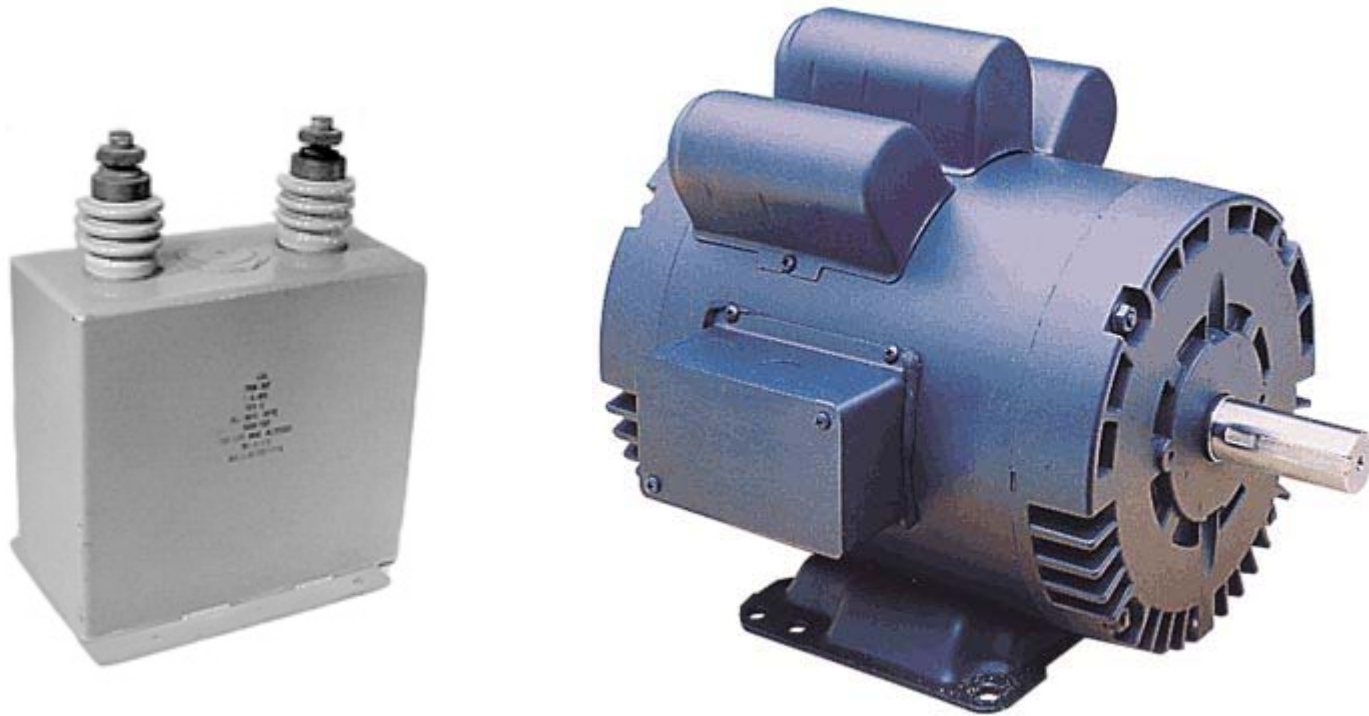As  $\varphi \downarrow$ ,  $\cos \varphi \uparrow$  and  $I \uparrow$




# Adding a Capacitor

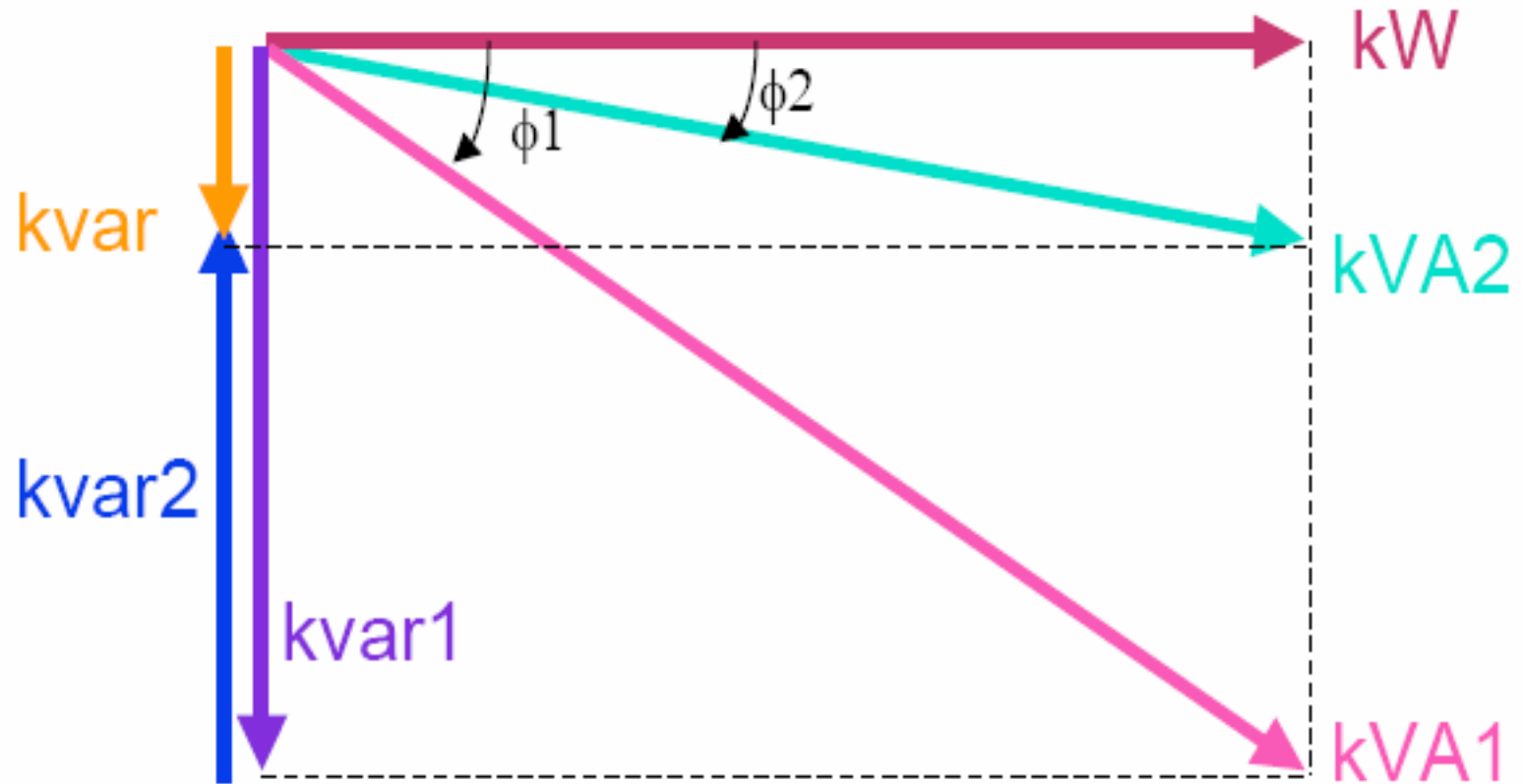


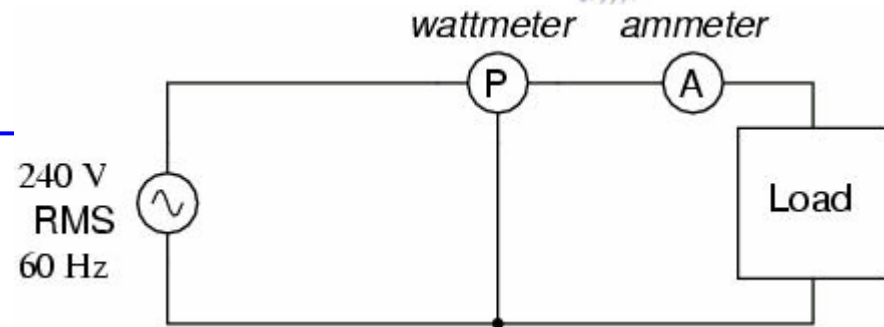
# Example

*Find pf and capacitor value to correct the pf.*




**Wattmeter reading = 1.5 kW**

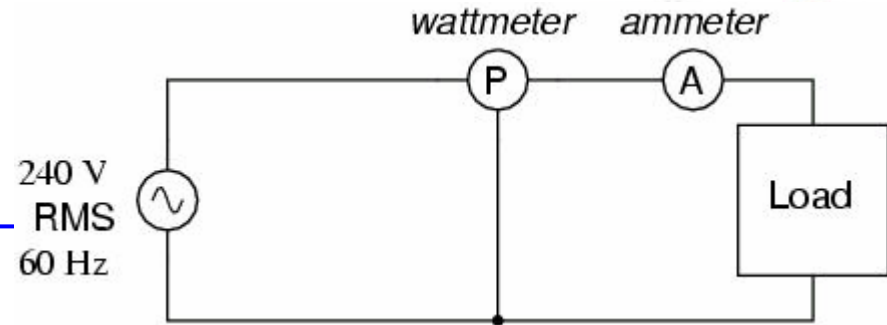**Ammeter reading = 9.615 A rms**

$$S = IE = (9.615\text{A})(240\text{V}) = 2.308 \text{ kVA}$$

$$\text{pf} = \frac{P}{S} = \frac{1.5\text{kW}}{2.308\text{kVA}} = 0.65$$






**Wattmeter reading = 1.5 kW**  
**Ammeter reading = 9.615 A rms**

$$Q_I = \sqrt{S^2 - P^2} = 1.754 \text{ kVAR}$$

$$X = E^2 / Q = 32.845$$
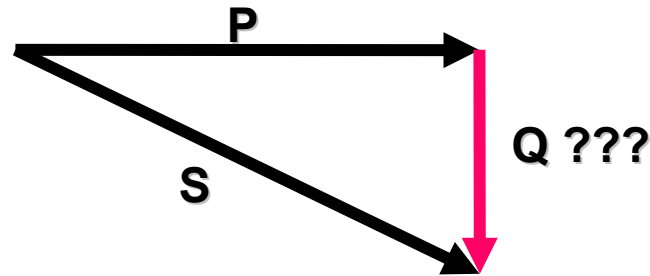
$$C = 1 / 2\pi f X_c = 80.761 \mu\text{F}$$



By calculating the current through the capacitor;

you will find that  $Q_c = 1.737 \text{ kVAR}$

Total kVAR =  $1.754 \text{ kVAR} - 1.737 \text{ kVAR} = 16.51 \text{ VAR}$

$$S_{\text{new}} = 1.50009 \text{ kVA}$$

$$\text{pf}_{\text{corrected}} = \frac{1.5 \text{ kW}}{1.50009 \text{ kVA}} = 0.99994 \text{ 😊}$$

# Results

---

- The corrected power factor is 0.99994
- The new total current is (1.50009 kVA / 240 Volts), or **6.25** amps vs. **9.615** amps for poor power factor!
- This lower total current will translate to less heat losses in the circuit wiring, meaning greater system efficiency (less power wasted).

# Easier Way to Find Capacitor Value

---

To properly select the amount of KVAR required to correct the lagging power factor of a 3-phase motor you must follow the steps as stated.

- **Step #1:** Determine KW and Existing Power Factor.
- **Step # 2:** Existing Power Factor on Table, move across table to Desired Power Factor. The number represented is your multiplier number.
- **Step #3:** Multiply KW by the multiplier of the Desired Power Factor.



# Notes

---

- ❑ For purely resistive circuits, pf is perfect “1”
- ❑ For purely inductive or capacitive circuits, pf is zero
- ❑ Poor pf can be corrected by adding a capacitor parallel to the circuit.
- ❑ The capacitor will have an opposite amount of the reactive power
- ❑ Too much capacitance will result in a low pf

# Advantages of Good pf:

---

- For the same active power taken by the load, the line current drawn from the network reduces
  - The lower total current will translate to a less heat losses in the circuit wiring, meaning greater system efficiency (less power wasted); therefore reduced energy costs
  - Life time of these devices increase
  - Penalties for bad “pf” are canceled
  - Electrical bill is reduced

- The significant effect of improving the power factor of a circuit is to reduce the current flowing through that circuit which in turn result in the following benefit, Less total plant KVA for the same KW working power

<b>POWER FACTOR</b>	<b>60%</b>	<b>70%</b>	<b>80%</b>	<b>90%</b>	<b>100%</b>
<b>REAL POWER (kW)</b>	<b>600</b>	<b>600</b>	<b>600</b>	<b>600</b>	<b>600</b>
<b>REACTIVE POWER (kVR)</b>	<b>800</b>	<b>612</b>	<b>450</b>	<b>291</b>	<b>0</b>
<b>TOTAL POWER (kVA)</b>	<b>1000</b>	<b>857</b>	<b>750</b>	<b>667</b>	<b>600</b>



# Power Factor Clause; DTE(D6.a)

---

- ❑ The rates and charges under this tariff are based on the customer maintaining a pf of not less than 85% lagging. Any pf less than 70% will not be permitted and the customer will be required to install at his own expense such as corrective equipment as may be necessary to improve pf. A penalty will be applied ..... Etc.
- ❑ DTE rates call for penalties ranging from 1 to 3% when power factor is between 85 and 70%.

# Measurement of Power Factor And Latest Technology

- ❑ Fluke 43B(one phase )
- ❑ Fluke 434 Power Quality Analyzer(3 phase)
- ❑ Fluke 40



# References

---

- ❑ <http://quest.deco.com/emd/orgs/majorAccountServices/techpro/login.html>
- ❑ <http://memonline.com/pfc1.html>
- ☑ <S:\EP Common\ABB Inc\ABB.2004.LVNO.Presentation>

---

Any Questions ?  
Thank you

